

Connor Aksama  
EE 371  
February 12, 2023  
Lab 4 Report

## Procedure

This lab is comprised of two tasks. The first task involved implementing a bit counting algorithm in hardware using a given ASMD chart. The second task involved designing a binary search algorithm using an ASMD chart, then implementing the algorithm in hardware.

### Task 1

I approached this task by first planning out the division between functionality in the controller and the datapath of the hardware implementation. I determined what signals would need to be output from the controller to the datapath, how those signals would affect the data flow, and what feedback would be sent back to the controller. The controller would handle FSM states and transitions, sending signals to the datapath module indicating which state it was currently in. The datapath module would then modify its internally stored data while outputting intermediate results and send feedback to the controller whether the process was complete or not.

After deciding what would be contained within each component of the system, these modules were implemented in Verilog, then simulated and verified using ModelSim.

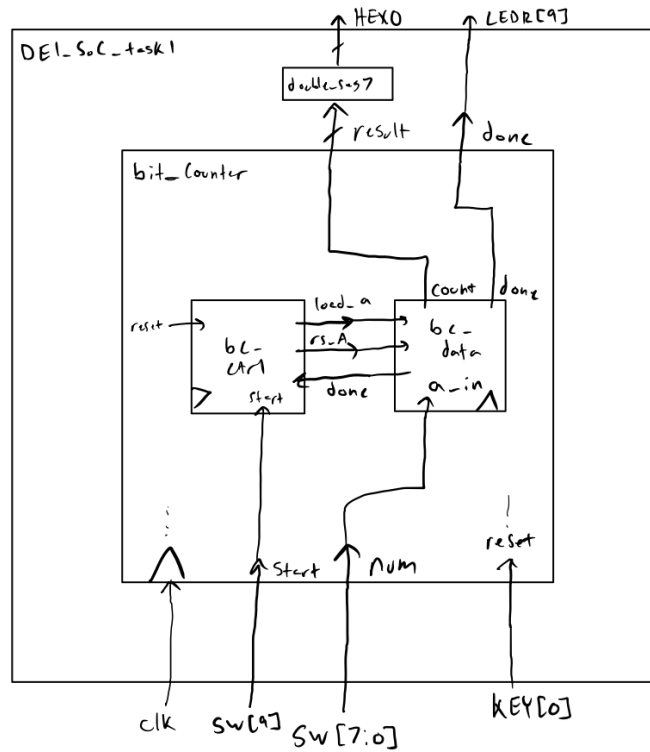


Figure 1. Top-Level Block Diagram for Lab 4 Task 1.

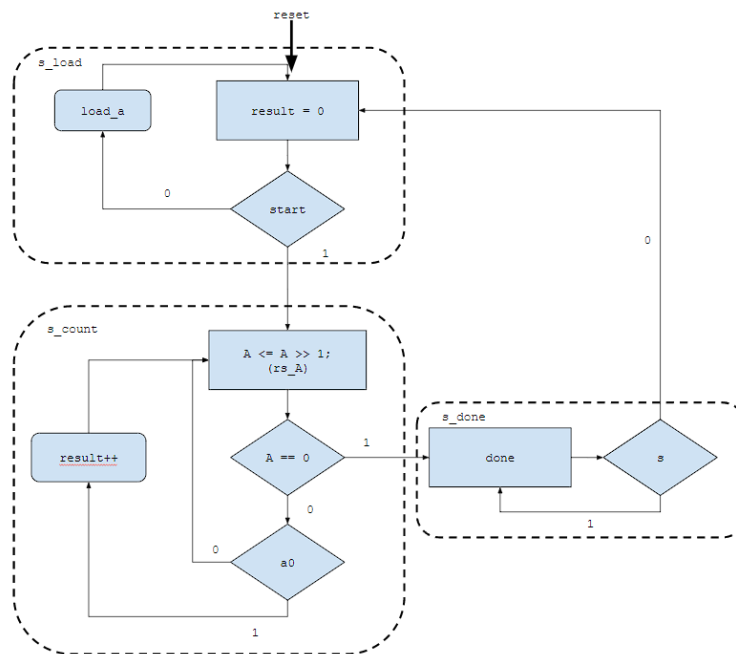


Figure 2. ASMD chart showing the bit counting algorithm.

## Task 2

I approached this task by first planning out the high-level algorithm for the binary search. I then drafted an ASM chart to detail each state and the decisions to make at each one. Next, I converted this chart to an ASMD chart by deciding how values would be stored in registers and thinking about when each register would hold a valid value at each state to determine FSM states and timing for transitions between states.

After this ASMD chart was created, similarly to Task 1, distinctions were made between what would belong in a controller module and a datapath module.

These modules were then implemented in Verilog, then tested and simulated in ModelSim before being uploaded and tested on hardware.

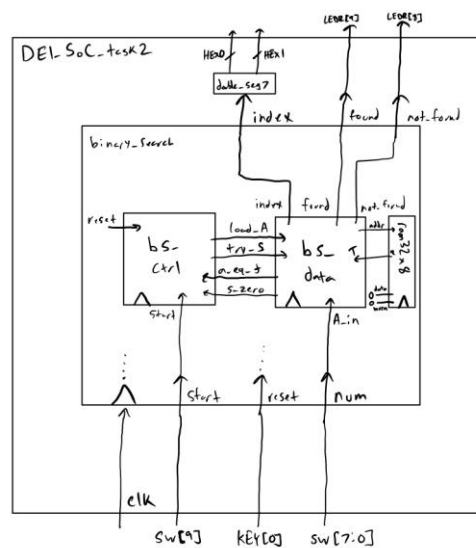


Figure 3. Top-Level Block Diagram for Lab 4 Task 2.

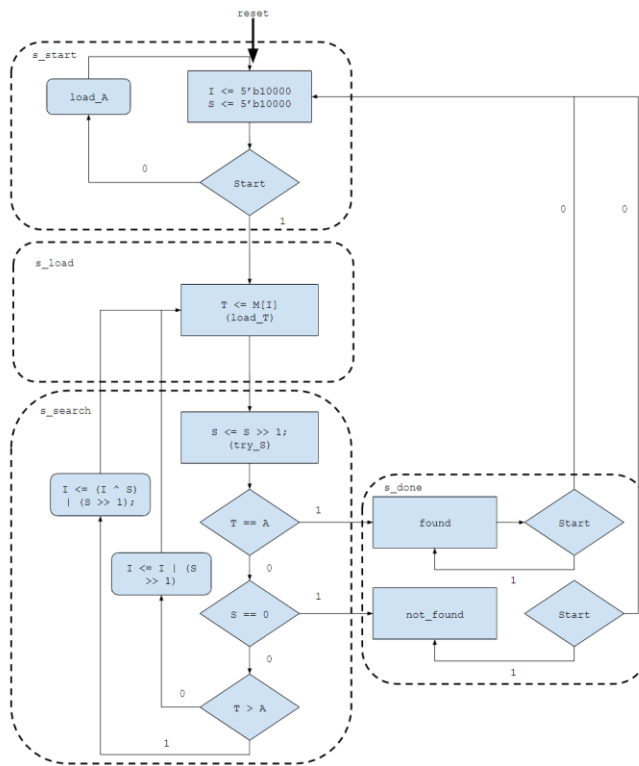


Figure 4. ASMD chart for the Lab 4 Task 2 Design.

## Results

### Task 1

The following are screenshots from ModelSim simulations for each module used in the bit counter design.

 


Figure 5. ModelSim Waveform for the Task 1 controller testbench.

This testbench shows the transitions between each of the states in the ASMD chart. After resetting, the system stays in the load state until the start signal is asserted. Following this, the load signal is raised until the done signal is asserted. After this, the controller remains idle until the start signal is lowered, at which point the controller returns to the start state.

 


Figure 6. ModelSim Waveform for the Task 1 datapath testbench.

This testbench shows how the internal data of the datapath module is manipulated given external signals from a controller module. While the load signal is asserted, the module samples the input number and holds the count at 0. Once the load signal is low and the right shift signal is high, the process of right shifting and counting bits begins and stops and outputs done once the internal number reaches 0 where it stays until the load signal is asserted again.

 


Figure 7. ModelSim Waveform for the Bit Counting module.

This testbench shows the behavior of the design with the controller and datapath modules connected. A number is loaded into the module with the start signal lowered with the result remaining at 0. Once the start signal is asserted, the result begins to increment until the final answer is reached. The system then stays at this state until start is lowered. At this point the next number is loaded in, the result reset, and the process begins again.

 


Figure 8. ModelSim Waveform for the Task 1 top-level design module

This testbench shows the correct functionality for the system when connected to the external ports of the board. The testing process is identical to the one shown in Figure 7, except with input and output signals coming from or going to the board's peripherals.

See Figure 13 for the testbench of the double seven-segment display module.

## Task 2

 


Figure 9. ModelSim Waveform for the Task 2 controller module.

This testbench illustrates the state transitions of the controller module in response to sample feedback from a connected datapath module. On reset, the module outputs the load signal. When the start signal is raised, the controller begins oscillating between a signal to try the current bit index (S) and loading in a value from RAM. Once the equality signal or the zero signal is raised, the controller goes idle until the start signal is lowered.

 


Figure 10. ModelSim Waveform for the Task 2 datapath module.

This testbench shows how data is manipulated in response to signals from a sample connected controller module. On a load signal, the input number is loaded. Then as input signals oscillate between signals to load a value from the connected RAM and to try the current bit index, the output result is shown being updated as the target value is being approached. If the value is found, the module outputs a found signal, and a not found signal otherwise.

 


Figure 11. ModelSim Waveform for the binary search module.

This testbench shows the behavior of the design with the controller and datapath modules connected. A number is loaded into the module with the start signal lowered with the result remaining at its start value. Once the start signal is asserted, the result begins to change until the search terminates. The

Timing diagram showing the relationship between LEDR[8], LEDR[9], and KEY[0]. The diagram shows a sequence of events where LEDR[8] and LEDR[9] are high, then LEDR[8] goes low, then LEDR[9] goes low, and finally KEY[0] is toggled. The signals are labeled with values like 0e, 79, 0, 1, 55, 1, 0.

This testbench shows the correct functionality for the system when connected to the external ports of the board. The testing process is identical to the one shown in Figure 11, except with input and output signals coming from or going to the board's peripherals.

ModelSim Hexadecimal Code	Seven Segment Display Character
40	0
79	1
24	2
30	3
19	4
12	5
02	6
78	7
00	8
10	9
08	A
03	b
27	c
21	d
06	E
0e	F

[illegible]

 


Figure 13. ModelSim Waveform for the Double Seven Segment Display module testbench.

This waveform demonstrates the two digit, hexadecimal display given any number from 0x00 to 0xff. Refer to Table 1 to decode the hexadecimal values to their corresponding characters.



## Final Product

The overarching goal of this lab was to gain experience designing, interpreting, and implementing ASMD charts. The main result of Task 1 was a module that implemented a bit counting algorithm using a given ASMD chart. This system would load in an 8-bit number inputted by a user via an array of switches, and when a start signal was triggered with another switch, the number of '1' bits in the number would be shown on the HEX display along with an LED signal indicating whether the process was complete or not.

In Task 2, a binary search algorithm was created using an ASMD chart, then implemented in hardware. This system would take in a target value inputted by a user via an array of switches, and when a start signal was triggered with another switch, the index of the target value in a preprogrammed RAM module would be shown on the HEX display along with LED signals indicating whether the value was successfully found in the RAM or not.

## Appendix: SystemVerilog Code

(See next page)

```

1  /*****
2
3  bc_ctrl.sv
4
5  *****/
6
7  /*
8   * Connor Aksama
9   * 02/12/2023
10  * CSE 371
11  * Lab 4
12  */
13
14  /**
15   * Controller module for the bit counting system.
16
17   * Inputs:
18   *     start [1 bit] - Signal to begin the binary searching process. While start is 0
19   *                     and the algo is not in progress,
20   *                     the input value num is loaded into the system. When start is 1,
21   *                     the algo begins. Once the search
22   *                     is complete, the next value of num will be loaded once start is
23   *                     lowered to 0.
24   *     done [1 bit] - 1 if the algo is complete, 0 o.w.
25   *     clk [1 bit] - The clock to use for this module.
26   *     reset [1 bit] - Resets the system to its initial state before the search process
27   *                     has started.
28
29   * Outputs:
30   *     load_A [1 bit] - 1 if A should be sampled from the user during this cycle, 0 o.w.
31   *     rs_A [1 bit] - 1 if the next bit of the num should be counted, 0 o.w.
32  */
33  module bc_ctrl (
34      output logic load_A, rs_A
35      ,input logic start, done, clk, reset
36      );
37
38      typedef enum logic [1:0] { s_load, s_count, s_done } state;
39
40      state ps, ns;
41
42      logic start_reg;
43
44      always_comb begin
45          // Handle state transitions
46          case (ps)
47              s_load: begin
48                  if (start_reg) begin
49                      ns = s_count;
50                  end else begin
51                      ns = s_load;
52                  end
53              end
54
55              s_count: begin
56                  if (done) begin
57                      ns = s_done;
58                  end else begin
59                      ns = s_count;
60                  end
61              end
62
63              s_done: begin
64                  if (!start_reg) begin
65                      ns = s_load;
66                  end else begin
67                      ns = s_done;
68                  end
69              end
70          endcase
71      end

```

```

66
67         endcase
68
69         // Control signals
70         load_A = (ps == s_load);
71         rs_A = (ps == s_count);
72
73     end
74
75     always_ff @(posedge clk) begin
76         // Register state, start
77         if (reset) begin
78             ps <= s_load;
79         end else begin
80             ps <= ns;
81         end
82
83         start_reg <= start;
84     end
85
86 endmodule // bc_ctrl
87
88 /*
89  * Testbench to test the functionality of the bc_ctrl module
90  */
91 module bc_ctrl_testbench();
92
93     logic start, done, clk, reset, load_A, rs_A;
94
95     bc_ctrl dut (.*);
96
97     parameter CLOCK_PERIOD = 100;
98     initial begin
99         clk <= 0;
100         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
101     end
102
103     initial begin
104         integer i;
105         // Hold in start state
106         @(posedge clk) reset <= 1'b1; start <= 1'b0; done <= 1'b0;
107         @(posedge clk); reset <= 1'b0;
108         @(posedge clk);
109
110         // Start algo
111         for (i = 0; i < 15; i++) begin
112             @(posedge clk) start <= 1'b1;
113         end
114
115         // Hold in done state
116         for (i = 0; i < 5; i++) begin
117             @(posedge clk) done <= 1'b1;
118         end
119
120         // Back to start state
121         start <= 1'b0;
122         for (i = 0; i < 5; i++) begin
123             @(posedge clk);
124         end
125
126         // Start algo
127         start <= 1'b1;
128         for (i = 0; i < 5; i++) begin
129             @(posedge clk);
130         end
131
132         $stop;
133     end
134

```

```

135 endmodule // bc_ctrl_testbench
136
137 /*****
138
139 bc_data.sv
140
141 *****/
142
143 /*
144  * Connor Aksama
145  * 02/12/2023
146  * CSE 371
147  * Lab 4
148  */
149
150 /**
151  * Datapath module for the bit counting system.
152
153  * Inputs:
154  *     a_in [8 bit] - The number to bit count. Latched when load_A is 1.
155  *     load_A [1 bit] - 1 if a_in should be sampled, 0 o.w.
156  *     rs_A [1 bit] - 1 if the next bit should be counted, 0 o.w.
157  *     clk [1 bit] - The clock to use for this module.
158
159  * Outputs:
160  *     done [1 bit] - 1 if the algo is complete, 0 o.w.
161  *     count [4 bit] - The number of 1s in the sampled a_in number. Valid if and only
162  *     if done is 1.
163  */
164 module bc_data (
165     output logic done
166     ,output logic [3:0] count
167     ,input logic load_A, rs_A, clk
168     ,input logic [7:0] a_in
169 );
170
171     logic [7:0] A;
172     logic [3:0] result;
173
174     always_ff @(posedge clk) begin
175         if (load_A) begin
176             // Sample A
177             result <= 4'b0;
178             A <= a_in;
179         end
180
181         if (rs_A) begin
182             // RS and count
183             A <= A >> 1;
184             if (A[0] == 1'b1) begin
185                 result <= result + 1'b1;
186             end
187         end
188
189         done <= (A == 0);
190         count <= result;
191     end
192 endmodule // bc_data
193
194 /**
195  * Testbench to test the functionality of the bc_data module.
196  */
197 module bc_data_testbench();
198
199     logic done, load_A, rs_A, clk;
200     logic [3:0] count;
201     logic [7:0] a_in;
202

```

```

203     bc_data dut (.*) ;
204
205     parameter CLOCK_PERIOD = 100;
206     initial begin
207         clk <= 0;
208         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
209     end
210
211     initial begin
212         integer i;
213         // Load value, hold in start
214         @(posedge clk) {load_A, rs_A} <= 2'b10; a_in <= 8'b10011111;
215         @(posedge clk);
216         @(posedge clk);
217         @(posedge clk);
218         @(posedge clk);
219         // Begin algo
220         for (i = 0; i < 15; i++) begin
221             @(posedge clk) {load_A, rs_A} <= 2'b01;
222         end
223         // Load value
224         @(posedge clk) {load_A, rs_A} <= 2'b10; a_in <= 8'b00000000;
225         @(posedge clk);
226         @(posedge clk);
227         @(posedge clk);
228         @(posedge clk);
229         // Begin
230         for (i = 0; i < 15; i++) begin
231             @(posedge clk) {load_A, rs_A} <= 2'b01;
232         end
233
234         $stop;
235     end
236
237 endmodule
238
239 /*****
240
241 bit_counter.sv
242
243 *****/
244
245 /*
246  * Connor Aksama
247  * 02/12/2023
248  * CSE 371
249  * Lab 4
250  */
251
252 /**
253  * Instantiates the controller and datapath modules and defines connections.
254
255  * Inputs:
256  *     num [8 bit] - Number to bit count.
257  *     start [1 bit] - Signal to begin the bit counting algo. While start is 0 and the
258  *                     algo is not in progress,
259  *                     the input value num is loaded into the system. When start is 1,
260  *                     the algo begins. Once the algo
261  *                     is complete, the next value of num will be loaded once start is
262  *                     lowered to 0.
263  *     clk [1 bit] - The clock to use for this module.
264  *     reset [1 bit] - Resets the system to its initial state before the algo has
265  *                     started.
266
267  * Outputs:
268  *     result [4 bit] - The number of 1s in the sampled num. This result value is valid if
269  *                     and only if done is raised.
270  *     If found and not_found are 0, the search is not complete.
271  *     done [1 bit] - 1 if the algo is complete, 0 o.w.

```

```

267  */
268  module bit_counter(
269      output logic [3:0] result
270      ,output logic done
271      ,input logic [7:0] num
272      ,input logic start, clk, reset
273  );
274
275      // Controller module
276      // In: start, done, clk, reset
277      // Out: load_A, rs_A
278      logic load_A, rs_A, d;
279      bc_ctrl controller (
280          .load_A(load_A)
281          ,.rs_A(rs_A)
282          ,.start(start)
283          ,.done(d)
284          ,.clk(clk)
285          ,.reset(reset)
286      );
287
288      // Datapath module
289      // In: load_A, rs_A, a_in, clk
290      // Out: done, count
291      bc_data datapath (
292          .done(d)
293          ,.count(result)
294          ,.load_A(load_A)
295          ,.rs_A(rs_A)
296          ,.a_in(num)
297          ,.clk(clk)
298      );
299
300      assign done = d;
301
302  endmodule // bit_counter
303
304  /*
305   * Testbench to test the functionality of the bit_counter module.
306   */
307  module bit_counter_testbench();
308
309      logic [3:0] result;
310      logic done;
311      logic [7:0] num;
312      logic start, clk, reset;
313
314      bit_counter dut (.*);
315
316      parameter CLOCK_PERIOD = 100;
317      initial begin
318          clk <= 0;
319          forever #(CLOCK_PERIOD / 2) clk <= ~clk;
320      end
321
322      initial begin
323          integer i;
324          // Load value
325          @(posedge clk) reset <= 1; num <= 8'b10000001; start <= 0;
326          @(posedge clk) reset <= 0;
327          @(posedge clk);
328          @(posedge clk);
329          @(posedge clk);
330          // Start count
331          @(posedge clk) start <= 1;
332
333          for (i = 0; i < 16; i++) begin
334              @(posedge clk);
335              end

```

```

336         // Load value
337         @(posedge clk) start <= 0; num <= 8'b0;
338         @(posedge clk);
339         @(posedge clk);
340         @(posedge clk);
341         // Start count
342         @(posedge clk) start <= 1;
343         for (i = 0; i < 5; i++) begin
344             @(posedge clk);
345         end
346
347         @(posedge clk);
348         @(posedge clk);
349
350         $stop;
351     end
352
353 endmodule // bit_counter_testbench
354
355 /*****
356
357 DE1_SoC_task1.sv
358
359 *****/
360
361 /*
362  * Connor Aksama
363  * 02/12/2023
364  * CSE 371
365  * Lab 4
366  */
367
368 /**
369  * Top-level module for Lab 4 Task 1. Instantiates binary search module and connects I/O
370  * to peripherals.
371
372  * Inputs:
373  *   SW [10 bit] - The 10 onboard switches, respectively.
374  *   KEY [4 bit] - The 4 onboard keys, respectively.
375  *   CLOCK_50 [1 bit] - The system clock to use for this module.
376
377  * Outputs:
378  *   HEX0 [7 bit] - Data to show on the HEX0 display, formatted in standard 7 segment
379  *   display format.
380  *   LEDR [10 bit] - Signal to output to 10 onboard LEDs, respectively.
381  */
382 module DE1_SoC_task1 (
383     output logic [6:0] HEX0
384     ,output logic [9:0] LEDR
385     ,input logic [3:0] KEY
386     ,input logic [9:0] SW
387     ,input logic CLOCK_50
388 );
389
390     // Bit counting module
391     // In: num, start, clk, reset
392     // Out: result, done
393     logic [3:0] result;
394     bit_counter bc (
395         .result(result)
396         ,.num(SW[7:0])
397         ,.done(LEDR[9])
398         ,.start(SW[9])
399         ,.clk(CLOCK_50)
400         ,.reset(~KEY[0])
401     );
402
403     // Seven-Segment display
404     // In: num

```



```

403         // Out: HEX0, HEX1(unused)
404         double_seg7 res_display (.HEX0(HEX0), .HEX1(), .num({4'b0, result}));
405
406     endmodule // DE1_SoC_task1
407
408     /*
409     * Testbench to test the functionality of the DE1_SoC_task1 module.
410     */
411     module DE1_SoC_task1_testbench();
412
413         logic [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5;
414         logic [9:0] LEDR;
415         logic [3:0] KEY;
416         logic [9:0] SW;
417         logic CLOCK_50, clk;
418
419         assign CLOCK_50 = clk;
420
421         DE1_SoC_task1 dut (.*);
422
423         parameter CLOCK_PERIOD = 100;
424         initial begin
425             clk <= 0;
426             forever #(CLOCK_PERIOD / 2) clk <= ~clk;
427         end
428
429         initial begin
430             integer i;
431
432             // Load value
433             @(posedge clk) KEY[0] <= 1'b0; SW[7:0] <= 8'b10000001; SW[9] <= 0;
434             @(posedge clk); KEY[0] <= 1'b1;
435             // Start count
436             @(posedge clk) SW[9] <= 1;
437
438             for (i = 0; i < 16; i++) begin
439                 @(posedge clk);
440             end
441             // Load value
442             @(posedge clk) SW[9] <= 0; SW[7:0] <= 8'b0;
443             @(posedge clk);
444             // Start count
445             @(posedge clk) SW[9] <= 1;
446             for (i = 0; i < 5; i++) begin
447                 @(posedge clk);
448             end
449
450             @(posedge clk);
451             @(posedge clk);
452
453             $stop;
454         end
455
456     endmodule // DE1_SoC_task1_testbench
457
458     /*****
459
460     double_seg7.sv
461
462     *****/
463
464     /*
465     * Connor Aksama
466     * 02/12/2023
467     * CSE 371
468     * Lab 4
469     */
470
471     /**

```

```

472 * Defines data for 2-digit hexadecimal HEX display given a 8-bit unsigned integer
473
474 * Inputs:
475 *     num [8 bit] - An unsigned integer value [0x0-0x7F] to display
476
477 * Outputs:
478 *     HEX0 [7 bit] - A HEX display for the least significant digit of the input num,
479 *     formatted in standard seven segment display format
480 *     HEX1 [7 bit] - A HEX display for the most significant digit of the input num,
481 *     formatted in standard seven segment display format
482 */
483 module double_seg7(
484     output logic [6:0] HEX0, HEX1
485     ,input logic [7:0] num
486 );
487
488 // Drive HEX output signals given num
489 always_comb begin
490     // Light HEX0 using LSD of num
491     case (num[3:0])
492         //      Light: 6543210
493         0: HEX0 = ~7'b0111111; // 0
494         1: HEX0 = ~7'b0000110; // 1
495         2: HEX0 = ~7'b1011011; // 2
496         3: HEX0 = ~7'b1001111; // 3
497         4: HEX0 = ~7'b1100110; // 4
498         5: HEX0 = ~7'b1101101; // 5
499         6: HEX0 = ~7'b1111101; // 6
500         7: HEX0 = ~7'b0000111; // 7
501         8: HEX0 = ~7'b1111111; // 8
502         9: HEX0 = ~7'b1101111; // 9
503         10: HEX0 = ~7'b1110111; // A
504         11: HEX0 = ~7'b1111100; // b
505         12: HEX0 = ~7'b1011000; // c
506         13: HEX0 = ~7'b1011110; // d
507         14: HEX0 = ~7'b1111001; // E
508         15: HEX0 = ~7'b1110001; // F
509     default: HEX0 = 7'bx;
510 endcase
511
512 // Light HEX1 using MSD of num
513 case (num >> 4)
514     //      Light: 6543210
515     0: HEX1 = ~7'b0111111; // 0
516     1: HEX1 = ~7'b0000110; // 1
517     2: HEX1 = ~7'b1011011; // 2
518     3: HEX1 = ~7'b1001111; // 3
519     4: HEX1 = ~7'b1100110; // 4
520     5: HEX1 = ~7'b1101101; // 5
521     6: HEX1 = ~7'b1111101; // 6
522     7: HEX1 = ~7'b0000111; // 7
523     8: HEX1 = ~7'b1111111; // 8
524     9: HEX1 = ~7'b1101111; // 9
525     10: HEX1 = ~7'b1110111; // A
526     11: HEX1 = ~7'b1111100; // b
527     12: HEX1 = ~7'b1011000; // c
528     13: HEX1 = ~7'b1011110; // d
529     14: HEX1 = ~7'b1111001; // E
530     15: HEX1 = ~7'b1110001; // F
531     default: HEX1 = 7'bx;
532 endcase
533
534 end
535
536 endmodule // double_seg7
537
538 /*
539 * Tests the functionality of the double_seg7 module.
540 */

```

```

539 module double_seg7_testbench();
540
541     logic [6:0] HEX0, HEX1;
542     logic [7:0] num;
543
544     double_seg7 dut (.HEX0, .HEX1, .num);
545
546     initial begin
547
548         integer i;
549
550         // Check HEX displays for integers 0x0-0xff
551         for (i = 0; i <= 8'hFF; i++) begin
552             #10 num = i;
553         end
554         #50;
555     end
556
557 endmodule // double_seg7_testbench
558
559 /*****
560
561 binary_search.sv
562
563 *****/
564
565 /*
566  * Connor Aksama
567  * 02/12/2023
568  * CSE 371
569  * Lab 4
570  */
571
572 /**
573  * Instantiates the controller and datapath modules and defines connections.
574
575  * Inputs:
576  *     num [8 bit] - An unsigned integer value to search for in the system's RAM.
577  *     start [1 bit] - Signal to begin the binary searching process. While start is 0
578  *                     and the search is not in progress,
579  *                     the input value num is loaded into the system. When start is 1,
580  *                     the search begins. Once the search
581  *                     is complete, the next value of num will be loaded once start is
582  *                     lowered to 0.
583  *     clk [1 bit] - The clock to use for this module.
584  *     reset [1 bit] - Resets the system to its initial state before the search process
585  *                     has started.
586
587  * Outputs:
588  *     index [5 bit] - The index of the given num in the system's RAM. This index value is
589  *                     valid if and only if found is raised.
590  *                     If found and not_found are 0, the search is not complete.
591  *     found [1 bit] - 1 if the search is complete and num was found in the system's RAM. 0
592  *                     otherwise.
593  *     not_found [1 bit] - 1 if the search is complete and num was not found in the
594  *                     system's RAM. 0 otherwise.
595  */
596 module binary_search (
597     output logic [4:0] index
598     ,output logic found, not_found
599     ,input logic [7:0] num
600     ,input logic start, clk, reset
601 );
602
603     // Controller Module
604     // In: a_eq_t, s_zero, start, clk, reset
605     // Out: load_A, try_S
606     logic load_A, try_S, a_eq_t, s_zero;
607     bs_ctrl controller (

```

```

601         .load_A(load_A)
602         ,.try_S(try_S)
603         ,.start(start)
604         ,.a_eq_t(a_eq_t)
605         ,.s_zero(s_zero)
606         ,.clk(clk)
607         ,.reset(reset)
608     );
609
610     // Datapath module
611     // In: A_in (user input), load_A, try_S (from controller), clk
612     // Out: index (answer), found, not_found (done & success?)
613     bs_data datapath (
614         .index(index)
615         ,.found(found)
616         ,.not_found(not_found)
617         ,.a_eq_t(a_eq_t)
618         ,.s_zero(s_zero)
619         ,.A_in(num)
620         ,.load_A(load_A)
621         ,.try_S(try_S)
622         ,.clk(clk)
623     );
624
625 endmodule // binary_search
626
627 /*
628  * The testbench module to test the functionality of the binary_search module.
629  */
630 `timescale 1 ps / 1 ps
631 module binary_search_testbench();
632
633     logic [4:0] index;
634     logic found, not_found;
635     logic [7:0] num;
636     logic start, clk, reset;
637
638     binary_search dut (.*);
639
640     parameter CLOCK_PERIOD = 100;
641     initial begin
642         clk <= 0;
643         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
644     end
645
646     initial begin
647         integer i;
648
649         @(posedge clk) reset <= 1'b1; start <= 1'b0; num <= 11;
650         @(posedge clk) reset <= 1'b0;
651         @(posedge clk);
652         @(posedge clk);
653         @(posedge clk) start <= 1'b1;
654
655         for (i = 0; i < 15; i++) begin
656             @(posedge clk);
657         end
658
659         @(posedge clk) start <= 1'b0; num <= 55;
660         @(posedge clk);
661         @(posedge clk);
662         @(posedge clk) start <= 1'b1;
663
664         for (i = 0; i < 15; i++) begin
665             @(posedge clk);
666         end
667         $stop;
668     end
669 end

```

```

670 endmodule // binary_search_testbench
671
672 /*****
673
674 bs_ctrl.sv
675
676 *****/
677
678 /*
679  * Connor Aksama
680  * 02/12/2023
681  * CSE 371
682  * Lab 4
683  */
684
685 /**
686  * Controller module for the binary search system.
687
688  * Inputs:
689  *     start [1 bit] - Signal to begin the binary searching process. While start is 0
690  *                    and the search is not in progress,
691  *                    the input value num is loaded into the system. When start is 1,
692  *                    the search begins. Once the search
693  *                    is complete, the next value of num will be loaded once start is
694  *                    lowered to 0.
695  *     a_eq_t [1 bit] - 1 if the search is complete and the number was found in RAM, 0
696  *                    o.w.
697  *     s_zero [1 bit] - 1 if the search is complete and the number was not found in
698  *                    RAM, 0 o.w.
699  *     clk [1 bit] - The clock to use for this module.
700  *     reset [1 bit] - Resets the system to its initial state before the search process
701  *                    has started.
702
703  * Outputs:
704  *     load_A [1 bit] - 1 if A should be sampled from the user during this cycle, 0 o.w.
705  *     try_S [1 bit] - 1 if the next bit index of the RAM address should be tested
706  *                    during this cycle, 0 o.w.
707  */
708 module bs_ctrl (
709     output logic load_A, try_S
710     ,input logic start, a_eq_t, s_zero, clk, reset
711 );
712
713     typedef enum logic [1:0] { s_start, s_load, s_search, s_done } state;
714
715     state ps, ns;
716
717     logic start_reg;
718
719     always_comb begin
720         // Handle state transitions
721         case (ps)
722             s_start: begin
723                 if (start_reg) begin
724                     ns = s_load;
725                 end else begin
726                     ns = s_start;
727                 end
728             end
729             s_load: begin
730                 ns = s_search;
731             end
732             s_search: begin
733                 if (a_eq_t | s_zero) begin
734                     ns = s_done;
735                 end else begin
736

```

```

732         ns = s_load;
733     end
734 end
735
736     s_done: begin
737         if (~start_reg) begin
738             ns = s_start;
739         end else begin
740             ns = s_done;
741         end
742     end
743
744 endcase
745
746 // Control signals to datapath
747 load_A = (ps == s_start);
748
749 try_S = (ps == s_search);
750 end
751
752 always_ff @(posedge clk) begin
753     // Register state and start input
754     if (reset) begin
755         ps <= s_start;
756     end else begin
757         ps <= ns;
758     end
759
760     start_reg <= start;
761 end
762
763 endmodule // bs_ctrl
764
765 /*
766  * Module to test the functionality of the bs_ctrl module
767  */
768 module bs_ctrl_testbench();
769
770     logic load_A, try_S;
771     logic start, a_eq_t, s_zero, clk, reset;
772
773     bs_ctrl dut (.*);
774
775     parameter CLOCK_PERIOD = 100;
776     initial begin
777         clk <= 0;
778         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
779     end
780
781     initial begin
782         integer i;
783
784         // Hold in start state
785         start <= 1'b0; a_eq_t <= 1'b0; s_zero <= 1'b0; reset <= 1'b1;
786         @(posedge clk) reset <= 1'b0;
787         @(posedge clk);
788         @(posedge clk);
789         @(posedge clk);
790         // Begin the search process
791         @(posedge clk) start <= 1'b1;
792
793         for (i = 0; i < 10; i++) begin
794             @(posedge clk);
795         end
796         // Search success
797         a_eq_t <= 1'b1;
798         // Hold in done state
799         for (i = 0; i < 5; i++) begin
800             @(posedge clk);

```

```

801     end
802     // Go back to start
803     start <= 1'b0; a_eq_t <= 1'b0; s_zero <= 1'b0;
804     for (i = 0; i < 5; i++) begin
805         @(posedge clk);
806     end
807     // Search
808     @(posedge clk) start <= 1'b1;
809
810     for (i = 0; i < 10; i++) begin
811         @(posedge clk);
812     end
813     // Search failure
814     s_zero <= 1'b1;
815     for (i = 0; i < 5; i++) begin
816         @(posedge clk);
817     end
818
819     $stop;
820 end
821
822 endmodule // bs_ctrl_testbench
823
824 /*****
825
826 bs_data.sv
827
828 *****/
829
830 /*
831  * Connor Aksama
832  * 02/12/2023
833  * CSE 371
834  * Lab 4
835  */
836
837 /**
838  * Datapath module for the binary search system.
839
840  * Inputs:
841  *     A_in [8 bit] - The number to search for in the RAM. Latched when load_A is true
842  *     load_A [1 bit] - 1 if A_in should be sampled, 0 o.w.
843  *     try_S [1 bit] - 1 if the next bit in the index should be tested, 0 o.w.
844  *     clk [1 bit] - The clock to use for this module.
845
846  * Outputs:
847  *     index [5 bit] - The index of the sampled A_in value in the RAM. Valid if and
848  *     only if found is 1.
849  *     a_eq_t [1 bit] - Feedback if the sampled A_in value is equal to the currently
850  *     read value from RAM. 1 if eq, 0 o.w.
851  *     s_zero [1 bit] - Feedback if all bits have been tested in the index. 1 if true,
852  *     0 o.w.
853  *     found [1 bit] - 1 if the search is complete and the sampled A_in was found in
854  *     RAM, 0 o.w.
855  *     not_found [1 bit] - 1 if the search is complete and the sampled A_in was not
856  *     found in RAM, 0 o.w.
857  */
858 module bs_data (
859     output logic [4:0] index
860     ,output logic a_eq_t, s_zero, found, not_found
861     ,input logic [7:0] A_in
862     ,input logic load_A, try_S, clk
863 );
864
865     logic [4:0] I, S;
866     logic [7:0] T, A;
867
868     // RAM block
869     // In: address/I(ndex), clk

```

```

865 // Out: data/wren - unused; q - data
866 ram32x8 ram (
867     .address(I)
868     ,.clock(clk)
869     ,.data(8'b0)
870     ,.wren(1'b0)
871     ,.q(T)
872 );
873
874 assign a_eq_t = (A == T);
875 assign s_zero = (S == '0);
876
877 always_ff @(posedge clk) begin
878
879     if (load_A) begin
880         S <= 5'b10000;
881         I <= 5'b10000;
882         A <= A_in;
883     end
884
885     if (try_S) begin
886         S <= S >> 1;
887         if (T > A) begin
888             I <= (I ^ S) | (S >> 1);
889         end else if (T < A) begin
890             I <= I | (S >> 1);
891         end
892     end
893
894     index <= I;
895     found <= (A == T);
896     not_found <= (A != T) & (S == 0);
897 end
898
899 endmodule // bs_data
900
901 /*
902  * Testbench to test the functionality of the bs_data module
903  */
904 `timescale 1 ps / 1 ps
905 module bs_data_testbench();
906
907     logic [4:0] index;
908     logic found, not_found, a_eq_t, s_zero;
909     logic [7:0] A_in;
910     logic load_A, try_S, clk;
911
912     bs_data dut (.*) ;
913
914     parameter CLOCK_PERIOD = 100;
915     initial begin
916         clk <= 0;
917         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
918     end
919
920     initial begin
921         integer i;
922
923         // Load value
924         A_in <= 13; load_A <= 1'b1; try_S <= 1'b0;
925
926         // Search
927         for (i = 0; i < 10; i++) begin
928             @(posedge clk); load_A <= 1'b0; try_S <= 1'b0;
929             @(posedge clk); load_A <= 1'b0; try_S <= 1'b1;
930         end
931
932         // Load
933         @(posedge clk) A_in <= 33; load_A <= 1'b1; try_S <= 1'b0;

```



```

934         // Search
935         for (i = 0; i < 10; i++) begin
936             @(posedge clk); load_A <= 1'b0; try_S <= 1'b0;
937             @(posedge clk); load_A <= 1'b0; try_S <= 1'b1;
938         end
939
940         $stop;
941
942     end
943
944 endmodule // bs_data_testbench
945
946 /*****
947
948 DE1_SoC_task2.sv
949
950 *****/
951
952 /*
953  * Connor Aksama
954  * 02/12/2023
955  * CSE 371
956  * Lab 4
957  */
958
959 /**
960  * Top-level module for Lab 4 Task 2. Instantiates binary search module and connects I/O
961  * to peripherals.
962  *
963  * Inputs:
964  *   SW [10 bit] - The 10 onboard switches, respectively.
965  *   KEY [4 bit] - The 4 onboard keys, respectively.
966  *   CLOCK_50 [1 bit] - The system clock to use for this module.
967  *
968  * Outputs:
969  *   HEX0 [7 bit] - Data to show on the HEX0 display, formatted in standard 7 segment
970  *   display format.
971  *   HEX1 [7 bit] - Data to show on the HEX1 display, formatted in standard 7 segment
972  *   display format.
973  *   LEDR [10 bit] - Signal to output to 10 onboard LEDs, respectively.
974  */
975 module DE1_SoC_task2 (
976     output logic [6:0] HEX0, HEX1
977     ,output logic [9:0] LEDR
978     ,input logic [9:0] SW
979     ,input logic [3:0] KEY
980     ,input logic CLOCK_50
981 );
982
983     assign LEDR[7:0] = 8'b0;
984
985     // Seven-Segment display
986     // In: num
987     // Out: HEX0, HEX1
988     logic [7:0] index;
989     double_seg7 addr (
990         .HEX0(HEX0)
991         ,.HEX1(HEX1)
992         ,.num(index)
993     );
994
995     // Binary search module
996     // In: num (switch input), start (switch), clk, reset (key)
997     // Out: index (final answer), found (success), not_found (failure)
998     binary_search bs (
999         .index(index)
1000         ,.found(LEDR[9])
1001         ,.not_found(LEDR[8])
1002         ,.num(SW[7:0])

```

```

1000         ,.start(SW[9])
1001         ,.clk(CLOCK_50)
1002         ,.reset(~KEY[0])
1003     );
1004
1005 endmodule // DE1_SoC_task2
1006
1007 /*
1008  * Testbench to test the functionality of the DE1_SoC_task2 module
1009  */
1010 `timescale 1 ps / 1 ps
1011 module DE1_SoC_task2_testbench();
1012
1013     logic [6:0] HEX0, HEX1;
1014     logic [9:0] LEDR;
1015     logic [9:0] SW;
1016     logic [3:0] KEY;
1017     logic CLOCK_50, clk;
1018
1019     assign CLOCK_50 = clk;
1020
1021     DE1_SoC_task2 dut (.*);
1022
1023     parameter CLOCK_PERIOD = 100;
1024     initial begin
1025         clk <= 0;
1026         forever #(CLOCK_PERIOD / 2) clk <= ~clk;
1027     end
1028
1029     initial begin
1030         integer i;
1031
1032         // Load num
1033         @(posedge clk) KEY[0] <= 1'b0; SW[9] <= 1'b0; SW[7:0] <= 8'b00001011;
1034         @(posedge clk) KEY[0] <= 1'b1;
1035         @(posedge clk);
1036         @(posedge clk);
1037         // Start
1038         @(posedge clk) SW[9] <= 1'b1;
1039         // Search
1040         for (i = 0; i < 15; i++) begin
1041             @(posedge clk);
1042         end
1043
1044         // Load
1045         @(posedge clk) SW[9] <= 1'b0; SW[7:0] <= 8'b00110111;
1046         @(posedge clk);
1047         @(posedge clk);
1048         // Start
1049         @(posedge clk) SW[9] <= 1'b1;
1050         // Search
1051         for (i = 0; i < 15; i++) begin
1052             @(posedge clk);
1053         end
1054         $stop;
1055     end
1056
1057 endmodule // DE1_SoC_task2_testbench
1058

```